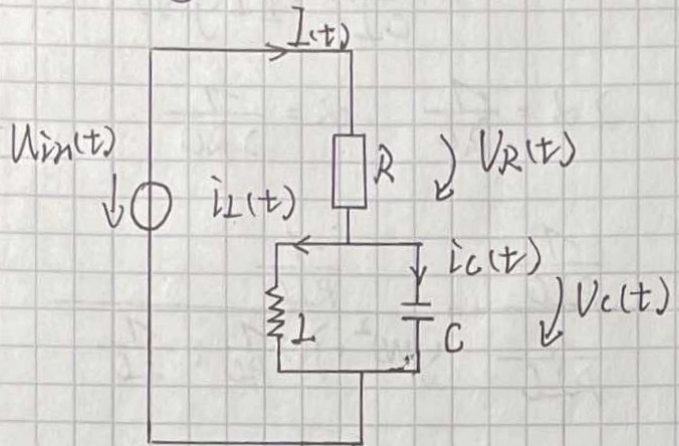



Aufgabe 2



Es gilt:

$$\begin{cases} I(t) = i_L(t) + i_C(t) \\ V_{in}(t) = V_R(t) + V_C(t) \\ V_C(t) = V_L(t) = V_C(t) \end{cases}$$

Ersatzschaltbild:

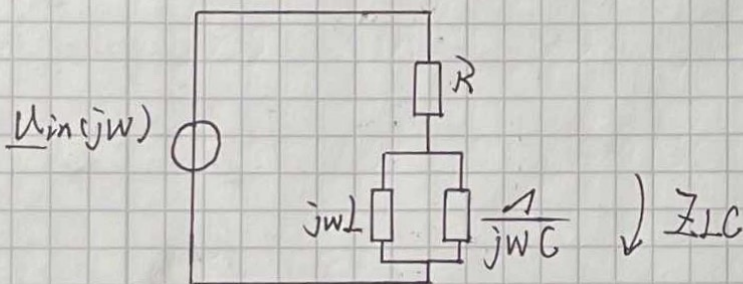

$$Z_{LC} = jwL \parallel \frac{1}{jwC}$$

$$= \frac{jwL \cdot \frac{1}{jwC}}{jwL + \frac{1}{jwC}} = \frac{L}{jwC L + \frac{1}{jw}} = \frac{jwL}{j^2 w^2 C L + 1}$$

$$\underline{I}_L(jw) \cdot jwL = \underline{I}_C(jw) \cdot \frac{1}{jwC}$$

$$\underline{I}_C(jw) + i_L(t) = \frac{V_{in}(jw)}{R + Z_{LC}}$$

$$\Rightarrow \frac{\underline{I}_L(jw)}{V_{in}(jw)} = \frac{1}{Z_{LC}(1 + j^2 w^2 LC)} = \frac{1}{jwL + j^2 w^2 RCL + R}$$



$$\Rightarrow \frac{1}{RCL} \cdot \underline{V_{in}}(j\omega) = \frac{1}{RC} \underline{i_L}(j\omega) \cdot j\omega + \underline{i_L}(j\omega) \cdot j^2\omega^2 + \frac{1}{CL} \cdot \underline{i_L}(j\omega)$$

$$\Rightarrow \omega_0^2 = \frac{1}{CL} \quad , \quad \omega_0 = \frac{1}{\sqrt{CL}} \quad , \quad 2\alpha = \frac{1}{RC} \quad , \quad \alpha = \frac{1}{2RC}$$

$$\underline{H}(j\omega) = \frac{1}{R + j\omega L + j^2\omega^2 RCL} \cdot \frac{\frac{1}{RLC}}{\frac{1}{RLC}} = \frac{\frac{1}{RLC}}{j\omega^2 + j\omega \frac{1}{RC} + \frac{1}{LC}}$$

$$\omega = 0 \Rightarrow \underline{H}(j\omega) = \frac{1}{R}$$

$$\omega \rightarrow \infty \Rightarrow \underline{H}(j\omega) = 0$$